



This circuit assumes a 12V supply for the 555 timer. Since you did not say otherwise, I also assume that that the 555 is set up as an Astable running at some frequency you have set. I don't know what the rest of your circuit looks like. If other voltage is used, you will need to adjust the resistors.

