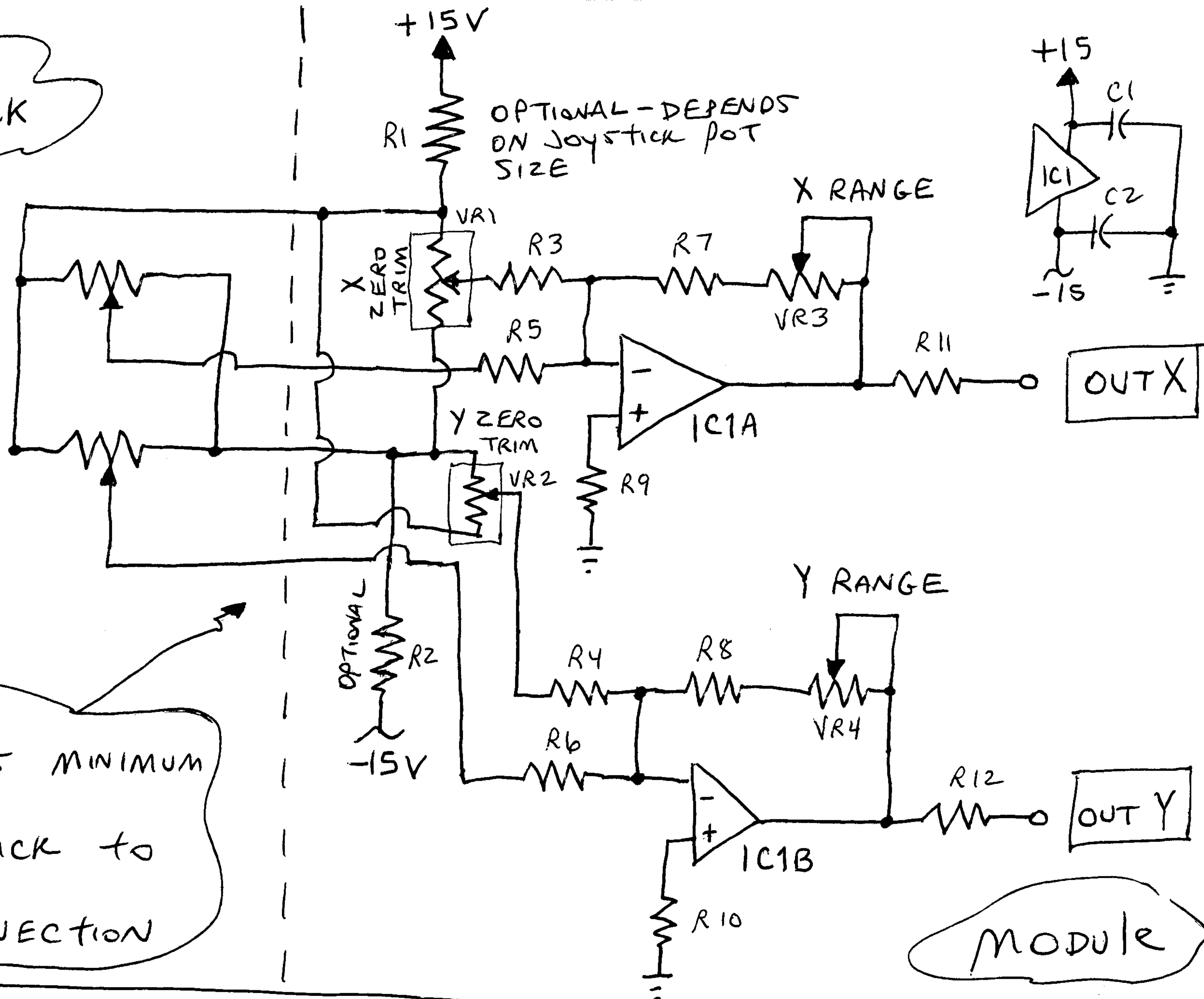


Joystick

X POT

Y POT

4 CONDUCTORS MINIMUM
FROM JOYSTICK TO
MODULE CONNECTION



MODULE

- PARTS:
- 1- DUAL OP AMP - LT1013 = BEST - ANY DECENT DUAL AMP LIKE TL072 OK
 - 2- RANGE POTS + KNOBS
 - 2- ZERO TRIM POTS
 - 10-12 - 1% RESISTORS
 - 2- CERAMIC CAPS
 - 1- SMALL PROTO PCB
 - TOTAL COST ABOUT \$10⁰⁰
 - ADD SUITABLE PANEL